

# Electricity & Safety Unit - Lesson 1

## Teachers Notes - Lesson 1 - Slide 19

**Simple Circuits Quiz Activity:** Ask your students to identify which circuits will make the light bulb glow.

**Which of these electrical circuits will make the light bulb glow?**

Correct answers: A & C

**Class discussion:**

- Ask some students to present their observations to the class.
- What circuits made the light bulb glow?
- What did the circuits that made the light bulb glow have in common?
- What did the circuits that didn't work have in common?

(Introduce the terms open and closed circuits)